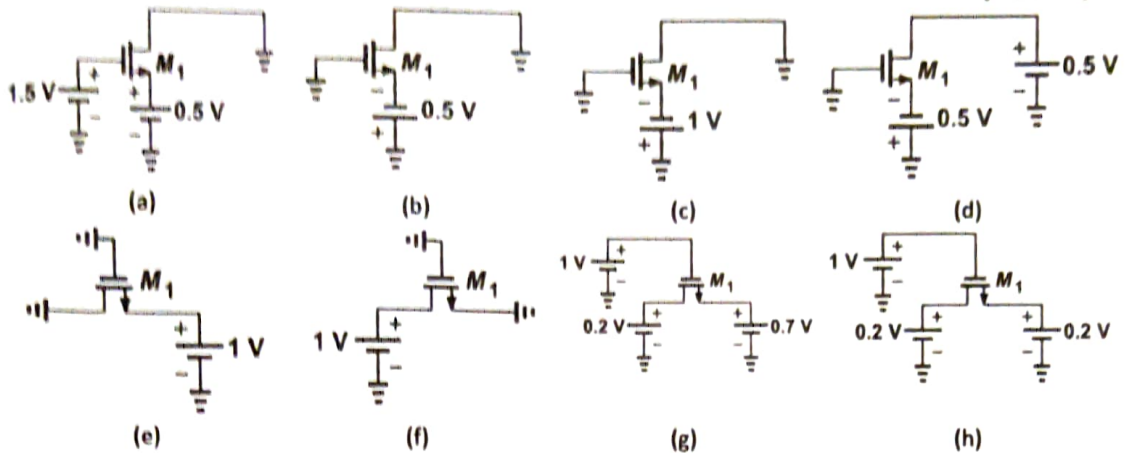



## Quiz-2: Analog Electronic Circuits (S25.EC2.103)

**NOTE:** No query allowed during the exam. Write your assumptions (if any) for each question.

**Q1.** Determine the region of operation of MOSFET ( $M_1$ ) in each of the circuits shown in Fig. below. [(a)-(h)]. Consider  $V_{TH}=0.4V$  [8 Marks]



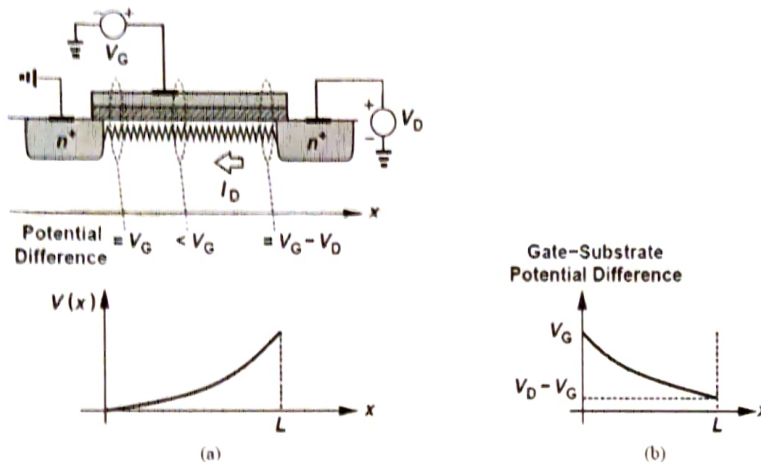**Q2.** Referring to Fig. Q2 below and assume  $V_D > 0$ , [5 Marks]



(a) Channel potential variation. (b) gate-substrate voltage difference along the channel.

Fig. Q2

- Sketch the electron density in the channel as a function of  $x$ .
- Sketch the local resistance of the channel (per unit length) as function of  $x$ .

**Q3 (a).** What is the effect of temperature on MOSFET. Discuss through the basic MOS equation, e.g. how your  $I_D$  get effected with rise in temperature when the MOSFET is in Saturation? [2 Marks]

**(b).** Pick the right option [(I)-(IV)] [4 Marks]

**(I).** The capacitances in MOSFET occurs due to \_\_\_\_\_

- Interconnects
- Difference in Doping concentration
- Difference in dopant materials
- All of the mentioned

**(II).** The parasitic capacitances found in MOSFET are \_\_\_\_\_

- Oxide related capacitances
- Inter electrode capacitance

- iii. Electrolytic capacitance
- iv. All of the mentioned

(III). In Cut-off region (assume MOS is in accumulation), the capacitance  $C_{gs}$  will be equal to

- i.  $2C_{GD0}$
- ii.  $C_{GS0} \cdot W$
- iii.  $C_{GB}$
- iv. All of the mentioned

(IV). In saturation mode operation, gate to drain capacitance (channel) is considered zero due to \_\_\_\_\_

- i. Gate and drain are interconnected
- ii. Channel length is reduced
- iii. Inversion layer doesn't exist
- iv. Drain is connected to ground

**Q4.** In the Fig.Q4, what is the minimum allowable value of  $V_{DD}$  if  $M_1$  must not enter the triode region?

Assume  $\lambda=0$ ,  $V_{TH}=0.4V$ ,  $\mu_n C_{ox}=200 \mu A/V^2$

[5 Marks]

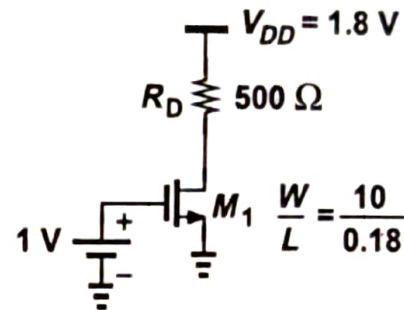


Fig. Q4

**Q5.** Sketch  $I_x$  as a function of  $V_x$  for the circuits shown in Fig. Q5. Assume  $V_x$  goes from 0 to  $V_{DD}=1.8V$ . Determine at what value of  $V_x$  the device changes its region of operation. Consider  $\lambda=0$ ,  $V_{TH}=0.4V$ .

[6 Marks]

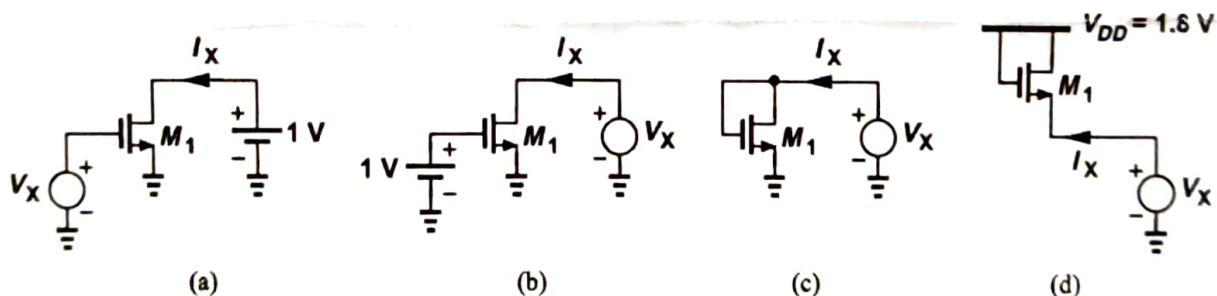


Fig. Q5