

End-Sem: Analog Electronic Circuits (S25.EC2.103)

Max. Marks: 80

Time: 3:00 PM-6:00 PM

Date: 29/04/2025

NOTE: No query allowed during the exam. Write your assumptions (if any) for each question.

Q1. A curious student like you decides to try a new circuit topology wherein the input is applied to the drain and the output is sensed at the source (Fig.1). Assume $\lambda \neq 0$, determine the voltage gain of the circuit and discuss the result. [10 Marks]

 


Fig.1

 


Fig.2

 


Fig.3

Q2(a). Discuss Miller theorem/effect in the context of amplifiers. How it impacts the amplifier performances? Prove that Miller effect results in an increase in the input capacitance (Just for reference; Fig.2 and Fig.3). [5 Marks]

(b). What is open-circuit time constant approach technique? Estimate the upper 3dB cut-off frequency of the given amplifiers (in Fig.4 and Fig.5) using open-circuit time constant approach. [10 Marks]

Assume $C_{gsn}=4fF$, $C_{gdn}=0.4fF$, $C_{dbn}=4fF$, $C_{gdp}=0.4fF$, $C_{dbp}=4fF$. Also, take the voltage gain of amplifiers equal to -8. What we call amplifier configurations in the given circuits (Fig.4 and Fig.5)?

[Hint: You may need to estimate the voltage gain at V_{o1} (Fig.5). Gain at this node will suffer from Miller effect. Just need to show gain at V_{o1} is ≤ 1]

 


Fig.4

 


Fig.5

Q 3(a). Consider the circuit shown in Fig.6. Calculate the maximum transconductance that M_1 can provide (without going into the triode region). Consider $V_{TH}=0.4V$ for NMOS. [5 Marks]

 


Fig.6

 


Fig.7

 


Fig.8

(b). Consider the circuit depicted in **Fig.7**, where $W/L = 20/0.18$. Assuming the current flowing through R_2 is one-tenth of I_{D1} , calculate the values of R_1 and R_2 so that $I_{D1} = 0.5$ mA. Consider $V_{TH} = 0.4$ V, $\mu_n C_{ox} = 200$ μ A/V² for NMOS. [5 Marks]

(c). The self-biased stage of **Fig.8** must be designed for a drain current of 1 mA. If M_1 is to provide a transconductance of $1/(100\Omega)$, calculate the required value of R_D . Consider $V_{TH} = 0.4$ V for NMOS.

[5 Marks]

Q4. The CS stage of **Fig. 9** must provide a voltage gain of 10 with a bias current of 0.5 mA. Assume $\lambda_1 = 0.1$ V⁻¹, and $\lambda_2 = 0.15$ V⁻¹. Consider $V_{TH} = 0.4$ V, $\mu_n C_{ox} = 200$ μ A/V² for the NMOS; $V_{TH} = -0.4$ V, $\mu_p C_{ox} = 100$ μ A/V² for the PMOS. [Hint: $r_0 = 1/\lambda I_D$] [2.5+2.5+5+5= 15 Marks]

(a). Compute the required value of $(W/L)_1$.

(b). if $(W/L)_2 = 20/0.18$, calculate the required value of V_B .

(c). if in the stage of Fig.9, M_2 has a long length so that $\lambda_2 \ll \lambda_1$. Calculate the voltage gain if $\lambda_1 = 0.1$ V⁻¹, $(W/L)_1 = 20/0.18$, and $I_D = 1$ mA.

(d). if the circuit of Fig.9 is designed for a bias current of I_1 with certain dimensions for M_1 and M_2 . If the width and the length of both transistors are doubled, how does the voltage gain change? Consider two cases: (i) the bias current remains constant, or (ii) the bias current is doubled.

 


Fig.9

Q5(a). The CG stage depicted in **Fig.10** must provide an input impedance of 50 Ω and an output impedance of 500 Ω . Assume $\lambda = 0$. Consider $V_{TH} = 0.4$ V, $\mu_n C_{ox} = 200$ μ A/V² for the NMOS.

[2+2+2=6Marks]

- What is the maximum allowable value of I_D ?
- With the value obtained in (a), calculate the required value of W/L .
- Compute the voltage gain.

(b). The source follower (CD amplifier) shown in **Fig.11** is biased through R_G . Calculate the voltage gain if $W/L = 20/0.18$ and $\lambda = 0.1$ V⁻¹. Consider $V_{TH} = 0.4$ V, $\mu_n C_{ox} = 200$ μ A/V² for the NMOS. [4 Marks]

 


Fig.10

 


Fig.11

Q6(a). Is there any trade-off between voltage gain and output voltage swing in MOS amplifier? Explain your answer through gain and voltage swing equations. You may consider resistive load common-source amplifier for your explanations. **[5 Marks]**

(b). Compare the common-source (CS), common-gate (CG), and common-drain (CD) amplifier configurations in terms of voltage gain, input impedance, output impedance, voltage swing, and frequency response in general. **[5 Marks]**


Q7. Draw a small-signal model of a common-source amplifier with **NMOS** active load, estimate voltage gain of this amplifier. Discuss the pros and cons of this amplifier. **[5 Marks]**

OR

 Q7. Find the output signal if the input is

- $V_{IN}=1V$ DC
- $V_{IN}=1V$ AC (very high frequency)

Assume the op-amp to be ideal. $R=100\ \Omega$, $C=1nF$ and $R'=500\ \Omega$



Note: Keep your answers to the point.

*******Best of luck*******